

## FSM Verilog HDL Coding

**FSM Coding Goals :** To determine what constitutes an efficient FSM coding style, we first need to identify HDL coding goals and why they are important. After the HDL coding goals have been identified, we can then quantify the capabilities of various FSM coding styles.

- The FSM coding style should be easily modified to change state encodings and FSM styles.
- The coding style should be compact.
- The coding style should be easy to code and understand.
- The coding style should facilitate debugging.
- The coding style should yield efficient synthesis results.


## FSM Verilog HDL Coding

One of the best Verilog coding styles is to code the FSM design using two always blocks, one for the sequential state register and one for the combinational next-state and combinational output logic.

### Two Always Block FSM Style (Good Style)?

```
module FSM (clk, rst, in, out) // module declaration
input clk; input in; input rst; output out; reg out;
reg [1:0] state; // State variable
reg [1:0] next_state; //Local variable
always @(posedge clk or posedge rst) //sequential state register
    if(rst)    state <= IDLE;
    else      state <= next_state;
always @(state or in) //combinational next state and output logic
    // compute next state and output logic whenever state or input changes
endmodule
```

# FSM Example1

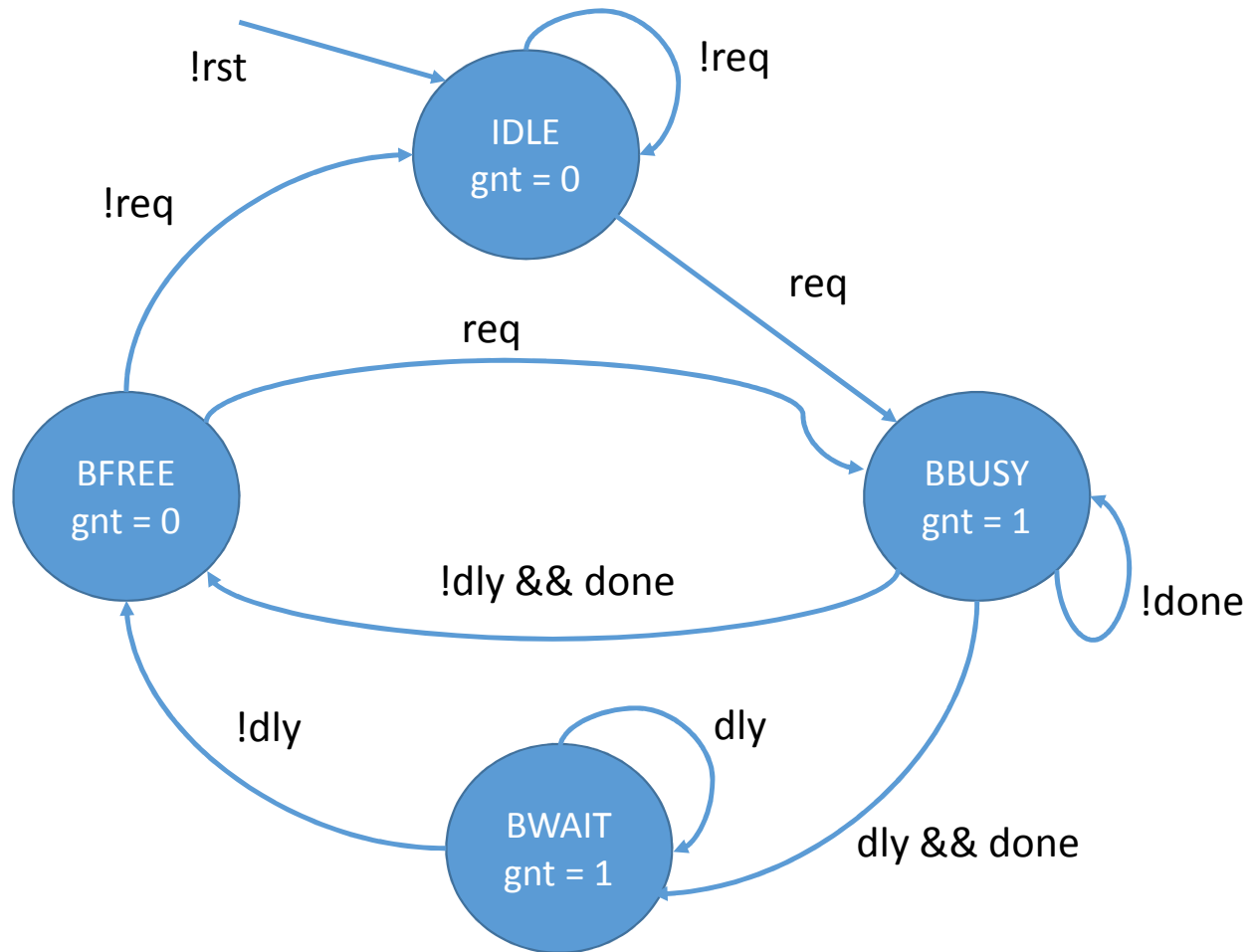


## FSM Example1: Coding using two always block

One of the best Verilog coding styles is to code the FSM design using two always blocks, one for the sequential state register and one for the combinational next-state and combinational output logic.

```
module fsm1 (output reg gnt, input
dly, done, req, clk, rst_n);
parameter [1:0] IDLE = 2'b00,
BBUSY = 2'b01,
BWAIT = 2'b10,
BFREE = 2'b11;
reg [1:0] state, next;
always @(posedge clk or negedge
rst_n)
    if (!rst_n)        state <= IDLE;
    else                state <= next;
```

Declarations are made for **state** and **next** (next state) after the parameter assignments.



## FSM Example1: Coding using two always block

```
always @(state or dly or done or req) begin
```

```
    next = 2'bx;
```

```
    gnt = 1'b0;
```

```
    case (state)
```

```
        IDLE : if (req) next = BBUSY;
```

```
            else next = IDLE;
```

```
        BBUSY: begin
```

```
            gnt = 1'b1;
```

```
            if (!done) next = BBUSY;
```

```
            else if ( dly) next = BWAIT;
```

```
            else next = BFREE;
```

```
        end
```

The combinational always block has a default **next** state assignment at the top of the always block

Default output assignments are made before coding the **case** statement (this eliminates latches and reduces the amount of code required to code the rest of the outputs in the **case** statement and highlights in the **case** statement exactly in which states the individual output(s) change).

## FSM Example1: Coding using two always block

```
BWAIT: begin
    gnt = 1'b1;
    if (!dly) next = BFREE;
    else next = BWAIT;
end
BFREE: if (req) next = BBUSY;
      else next = IDLE;
endcase
end
endmodule
```

## FSM Example1: Coding using one always block

```
module fsm1 (output reg gnt,  
input dly, done, req, clk, rst_n);  
parameter [1:0] IDLE = 2'd0,  
BBUSY = 2'd1,  
BWAIT = 2'd2,  
BFREE = 2'd3;  
reg [1:0] state;  
always @(posedge clk or negedge rst_n)  
    if (!rst_n) begin  
        state <= IDLE;  
        gnt <= 1'b0;  
    end  
    else begin  
        state <= 2'bx;  
        gnt <= 1'b0;  
        case (state)  
            IDLE : if (req) begin  
                state <= BBUSY;  
                gnt <= 1'b1;  
            end  
            else state <= IDLE;  
            BBUSY: if (!done) begin  
                state <= BBUSY;  
                gnt <= 1'b1;  
            end  
            else if ( dly) begin  
                state <= BWAIT;  
                gnt <= 1'b1;  
            end  
            else state <= BFREE;
```

## FSM Example1: Coding using one always block

```
BWAIT: if ( dly) begin
    state <= BWAIT;
    gnt <= 1'b1;
end
else state <= BFREE;
BFREE: if (req) begin
    state <= BBUSY;
    gnt <= 1'b1;
end
else state <= IDLE;
endcase
end
endmodule
```



# FSM Example1: One hot FSM Coding Style (Good Style)

Efficient (small and fast) onehot state machines can be coded using an inverse case statement; a case statement where each case item is an expression that evaluates to true or false.

```
module fsm1(output reg gnt,  
input dly, done, req, clk, rst_n);  
parameter [3:0] IDLE = 0,  
BBUSY = 1,  
BWAIT = 2,  
BFREE = 3;  
reg [3:0] state, next;  
always @(posedge clk or negedge rst_n)  
if (!rst_n) begin  
    state <= 4'b0;  
    state[IDLE] <= 1'b1;  
end  
else state <= next;
```

**Index into the state register,  
not state encodings**

**Onehot requires larger  
declarations**

**Reset modification**

# FSM Example1: One hot FSM Coding Style (Good Style)

always @(state or dly or done or req) begin

next = 4'b0; **Must make all-0's assignment**

gnt = 1'b0;

case (1'b1) // ambit synthesis case = full, parallel **Add "full" & "parallel" case**

**case (1'b1)**

state[IDLE] : if (req) next[BBUSY] = 1'b1;

else next[IDLE] = 1'b1;

state[BBUSY]: begin

gnt = 1'b1;

if (!done) next[BBUSY] = 1'b1;

else if ( dly) next[BWAIT] = 1'b1;

else next[BFREE] = 1'b1;

**Only update the  
next[next state] bit**

**state[current\_state]  
case items**

end

## FSM Example1: One hot FSM Coding Style (Good Style)

```
state[BWAIT]: begin
    gnt = 1'b1;
    if (!dly) next[BFREE] = 1'b1;
    else next[BWAIT] = 1'b1;
end
state[BFREE]: begin
    if (req) next[BBUSY] = 1'b1;
    else next[IDLE] = 1'b1;
end
endcase
end
endmodule
```

## FSM Example1: Registered FSM Outputs (Good Style)

Registering the outputs of an FSM design insures that the outputs are glitch-free and frequently improves synthesis results by standardizing the output and input delay constraints of synthesized modules. FSM outputs are easily registered by adding a third always sequential block to an FSM module where output assignments are generated in a case statement with case items corresponding to the next state that will be active when the output is clocked.

```
module fsm1(output reg gnt,  
input dly, done, req, clk, rst_n);  
parameter [1:0] IDLE = 2'b00,  
BBUSY = 2'b01,  
BWAIT = 2'b10,  
BFREE = 2'b11;  
reg [1:0] state, next;  
always @(posedge clk or negedge rst_n) // First always block  
    if (!rst_n) state <= IDLE;  
    else state <= next;
```

## FSM Example1: Registered FSM Outputs (Good Style)

always @(state or dly or done or req) begin // Second always block

next = 2'bx;

case (state)

    IDLE : if (req) next = BBUSY;

          else next = IDLE;

    BBUSY: if (!done) next = BBUSY;

          else if ( dly) next = BWAIT;

          else next = BFREE;

    BWAIT: if (!dly) next = BFREE;

          else next = BWAIT;

    BFREE: if (req) next = BBUSY;

          else next = IDLE;

endcase

end

## FSM Example1: Registered FSM Outputs (Good Style)

always @(posedge clk or negedge rst\_n) **// Third always block**

if (!rst\_n) gnt <= 1'b0;

else

begin

gnt <= 1'b0;

case (next)

IDLE, BFREE: ; // default outputs

BBUSY, BWAIT: gnt <= 1'b1;

endcase

end

endmodule


## FSM Example1: Compare each Coding Effort

Coding Style	Two always block coding style	One always block coding style (12%-83% larger)	Oneshot, two always block coding style	Three always block coding style w/ registered outputs
fsm1 (4 states, simple)	37 lines of code	47 lines of code (12%-27% larger)	42 lines of code	40 lines of code

we see that the one always block FSM coding style is the least efficient coding style with respect to the amount of RTL code required to render an equivalent design. In fact, the more outputs that an FSM design has and the more transition arcs in the FSM state diagram, and thus the faster the one always block coding style increases in size over comparable FSM coding styles.
 
## Example2: Detect input sequence 1101


The sequence detector will produce an output 1 whenever the input sequence 1101 occurs.




din	1	0	1	1	0	1	1	0	1	0	0	1	1	0	1	0
dout	0	0	0	0	0	1	0	0	1	0	0	0	0	0	1	0



 State Diagram to Detect input sequence 1101



 
## Detect input sequence 1101: Fsm Coding



```
// Sequence detector to Detect 1101 sequence
module seqdet(clk, rst, din, dout);
    input      clk, rst, din;
    output     dout;
    reg        dout;
```
 
## Example2: Detect input sequence 1101


```
reg[2:0] present_state, next_state;
```



```
parameter S0 = 3'b000, S1 = 3'b001, S11 = 3'b010,  
            S110 = 3'b011, S1101 = 3'b100;
```
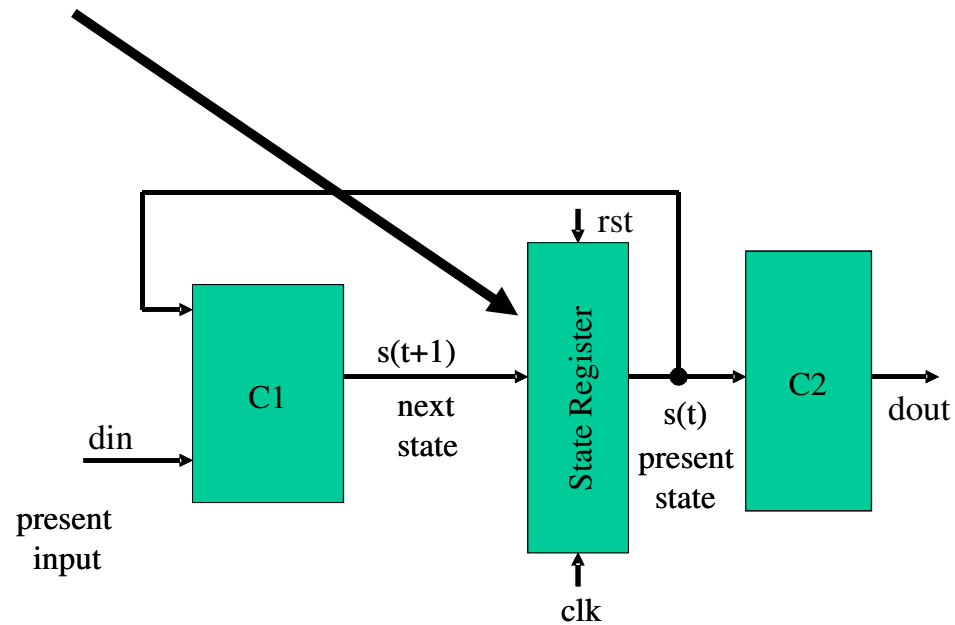
## Example2: Detect input sequence 1101

```
always @(posedge clk or posedge rst)
begin
    if (rst == 1)
        present_state <= S0;
    else
        present_state <= next_state;
end
```



## Example2: Detect input sequence 1101

```
// C1: Next State
always @(present_state or din)
begin
    case(present_state)
        S0: if(din == 1)
            next_state = S1;
            else next_state = S0;
        S1: if(din == 1)
            next_state = S11;
            else next_state = S0;
        S11: if(din == 0)
            next_state = S110;
            else next_state = S11;
        S110: if(din == 1)
            next_state = S1101;
            else next_state = S0;
        S1101: if(din == 0)
            next_state = S0;
            else next_state = S11;
        default next_state = S0;
    endcase
end
```

## Example2: Detect input sequence 1101

```
// C2: Outputs
```

```
always @(present_state)
```

```
begin
```

```
if(present_state == S1101)
```


```
    dout = 1;
```

```
else
```

```
    dout = 0;
```

```
end
```


```
endmodule
```

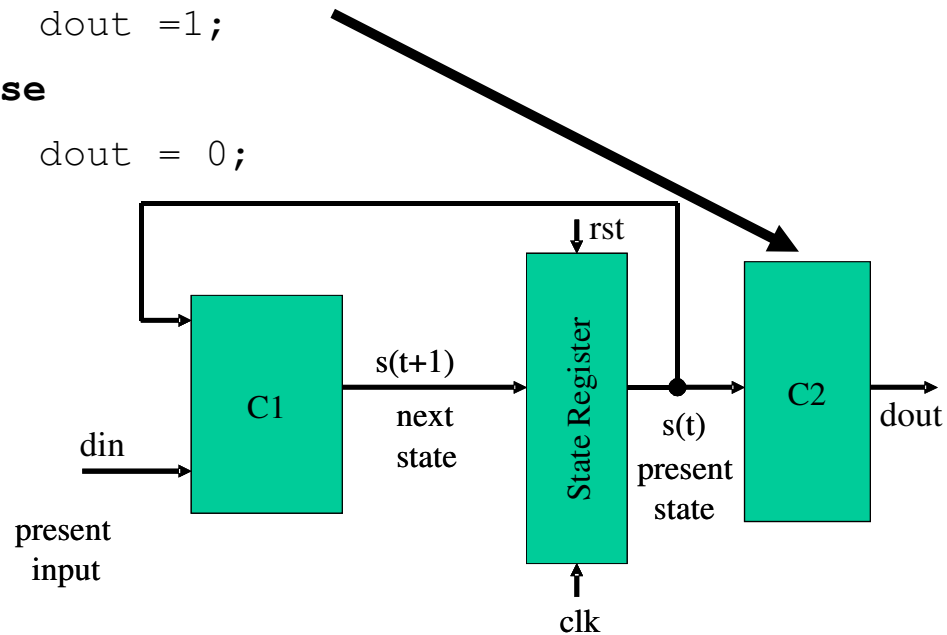
 
## Example3: FSM for an Arbiter

Lets take a simple arbiter as the example; this has got two request inputs and two grant outputs, as shown in the signal diagram.

- When req\_0 is asserted, gnt\_0 is asserted
- When req\_1 is asserted, gnt\_1 is asserted
- When both req\_0 and req\_1 are asserted then gnt\_0 is asserted i.e. higher priority is given to req\_0 over req\_1.




## Example3: State Diagram Of Arbiter

**IDLE** : In this state FSM waits for the assertion of req\_0 or req\_1 and drives both gnt\_0 and gnt\_1 to inactive state (low). This is the default state of the FSM, it is entered after the reset and also during fault recovery condition.

**GNT0** : FSM enters this state when req\_0 is asserted, and remains here as long as req\_0 is asserted. When req\_0 is de-asserted, FSM returns to the IDLE state.

 **GNT1** : FSM enters this state when req\_1 is asserted, and remains there as long as req\_1 is asserted. When req\_1 is de-asserted, FSM returns to the IDLE state





## Example3: FSM Coding

```
module fsm( clock, reset, req_0, req_1, gnt_0, gnt_1);
input  clock,reset,req_0,req_1;
output gnt_0,gnt_1;
wire  clock,reset,req_0,req_1;
reg   gnt_0,gnt_1;
parameter SIZE = 3      ;
parameter IDLE = 3'b001,GNT0 = 3'b010,GNT1 = 3'b100;
reg  [SIZE-1:0]  state    ;// Seq part of the FSM
reg  [SIZE-1:0]  next_state ;// combo part of FSM
//-----Code startes Here-----
always @ (state or req_0 or req_1)
begin : FSM_COMBO
    next_state = 3'b000;
    case(state)
        IDLE : if (req_0 == 1'b1) begin
                    next_state = GNT0;
                end else if (req_1 == 1'b1) begin
                    next_state= GNT1;
                end else begin
                    next_state = IDLE; end
        GNT0 : if (req_0 == 1'b1) begin
                    next_state = GNT0;
                end else begin
                    next_state = IDLE; end
        GNT1 : if (req_1 == 1'b1) begin
                    next_state = GNT1;
                end else begin
                    next_state = IDLE; end
        default : next_state = IDLE; endcase end
    end
end
```

## Example3: FSM Coding

```
always @ (posedge clock) // sequential logic
```

```
begin : FSM_SEQ
```

```
if (reset == 1'b1) begin
```

```
    state <= #1 IDLE;
```

```
end else begin
```

```
    state <= #1 next_state; end
```

```
end
```

```
//-----Output Logic-----
```

```
always @ (posedge clock)
```

```
begin : OUTPUT_LOGIC
```

```
if (reset == 1'b1) begin
```

```
    gnt_0 <= #1 1'b0;
```

```
    gnt_1 <= #1 1'b0;
```

```
end
```

```
else begin
```

```
case(state)
```

```
    IDLE : begin
```

```
        gnt_0 <= #1 1'b0; gnt_1 <= #1 1'b0;
```

```
    end
```

```
    GNT0 : begin
```

```
        gnt_0 <= #1 1'b1; gnt_1 <= #1 1'b0;
```

```
    end
```

```
    GNT1 : begin
```

```
        gnt_0 <= #1 1'b0; gnt_1 <= #1 1'b1;
```

```
    end
```

```
    default : begin
```

```
        gnt_0 <= #1 1'b0; gnt_1 <= #1 1'b0;
```

```
    end
```

```
endcase
```

```
end end endmodule
```