

EE-461 Assignment No-4

1. Write Verilog code for 4-bit Synchronous up counter and its test bench that will count in the sequence as shown below. Simulate using Modesim , take the waveform snap shot and submit as pdf in the portal.

